


# Chapter 2 – Basic Circuit Elements and Circuit Analysis

## Section 2: Circuit Analysis


**W. D. Prasad**
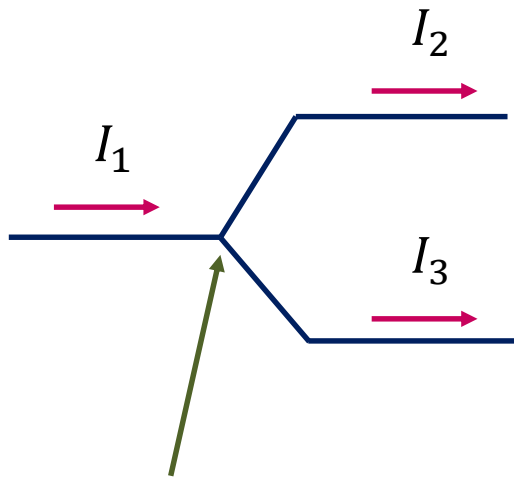
# Kirchhoff Laws

- Gustav Kirchhoff developed two fundamental laws which are used as a basis for analysis of all the circuits.
- The first law is based on the “Principle of conservation of charge”.



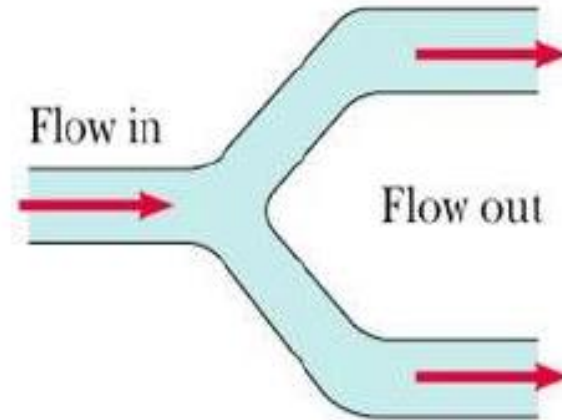A node is a point at which two or more circuit elements are connected




- What is the relationship between  $I_1$ ,  $I_2$ , and  $I_3$ ?

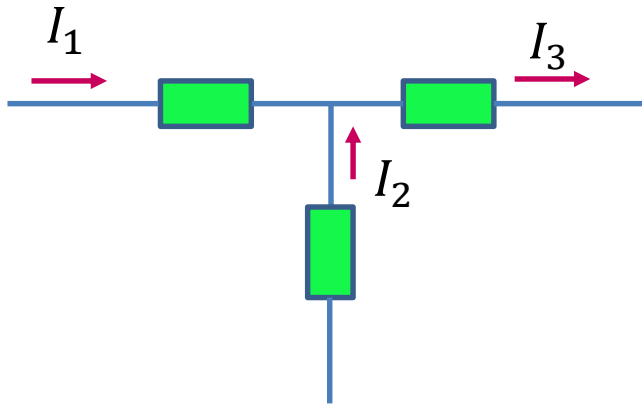
# Kirchhoff Current Law (KCL)

- KCL states that the algebraic sum of all the currents entering and leaving a node is zero.


$$\sum_{in} I = \sum_{out} I \quad \rightarrow \quad \sum_{node} I = 0$$


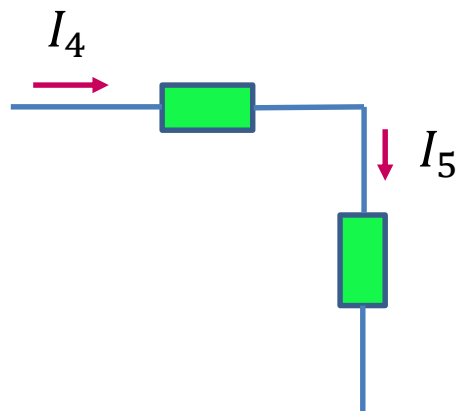
$$I_1 + I_2 + (-I_3) = 0$$
$$I_1 + I_2 = I_3$$




$$I_4 + (-I_5) = 0$$
$$I_4 = I_5$$

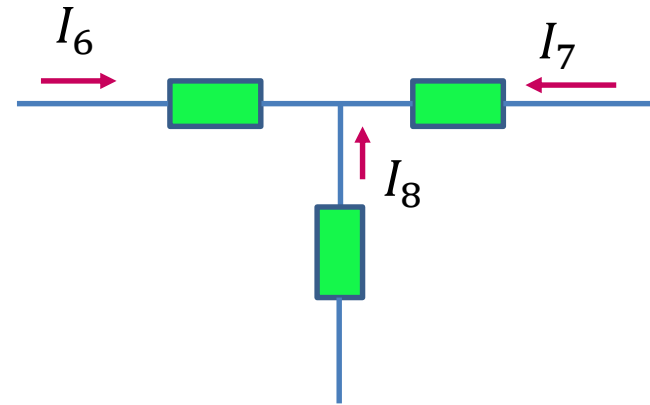

$$I_6 + I_7 + I_8 = 0$$

# Kirchhoff Current Law (KCL)

- Example:

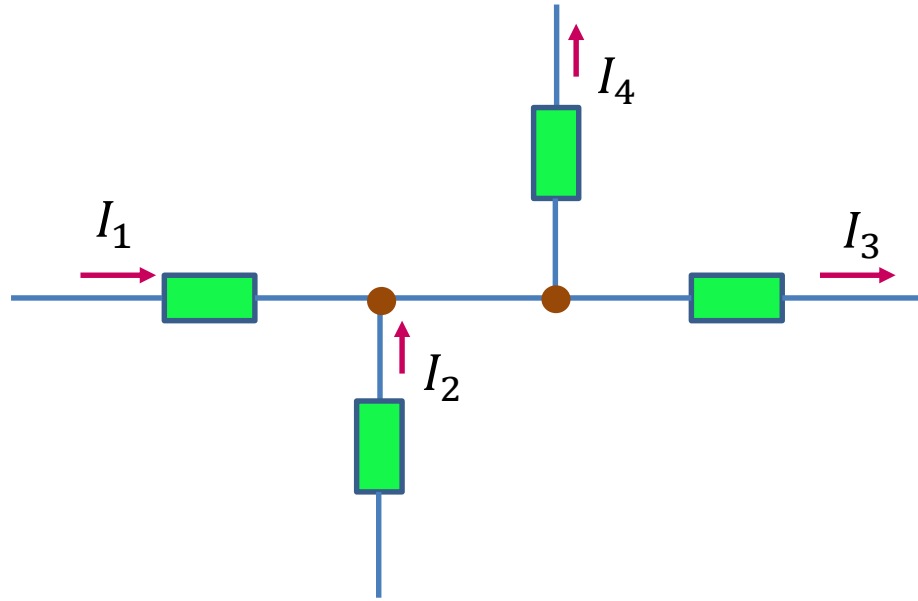


$$I_1 + I_2 + (-I_3) + (-I_4) = 0$$
$$I_1 + I_2 = I_3 + I_4$$

- All points in a circuit that are connected directly by ideal conductors can be considered to be a single node.
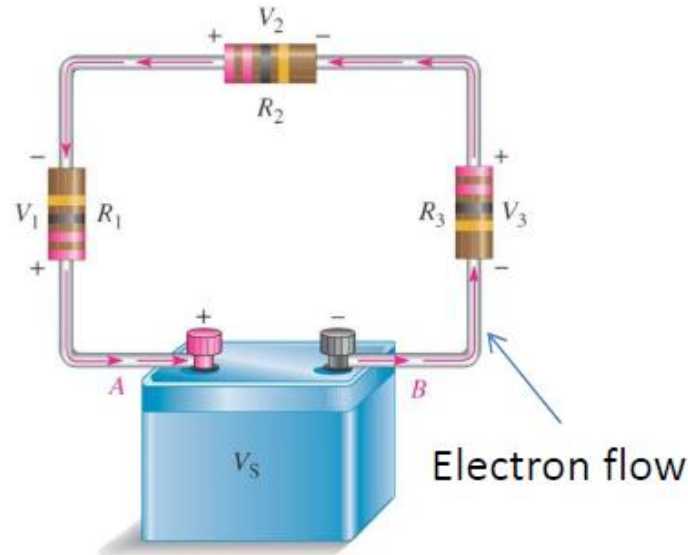
# Kirchhoff Laws

- Case study: three resistors connected in series across a voltage source.




- When electrons flow through a resistor, they lose energy and are therefore at a lower energy level when they emerge.
- This drop in energy level creates a potential difference or voltage drop.
- Due to conservation of energy, the voltage from point A to point B (the source voltage) must be the same as the sum of the series resistor voltage drops.

$$V_s = V_1 + V_2 + V_3$$

# Kirchhoff Voltage Law (KVL)

- Algebraic sum of voltages around any closed path (loop) in an electrical circuit equals zero.


$$\sum_{\text{loop}} v = 0$$

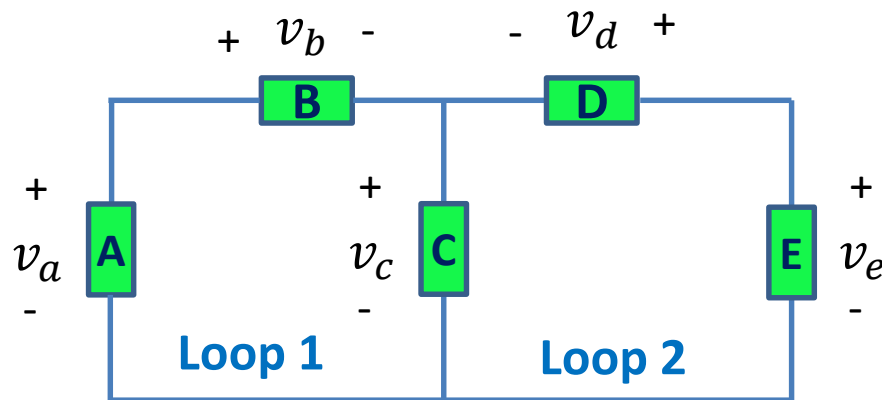

$$\text{Loop 1} \rightarrow v_a + (-v_b) + (-v_c) = 0 \rightarrow v_a = v_b + v_c$$

$$\text{Loop 2} \rightarrow v_c + v_d + (-v_e) = 0 \rightarrow v_e = v_c + v_d$$

# Voltage division principle

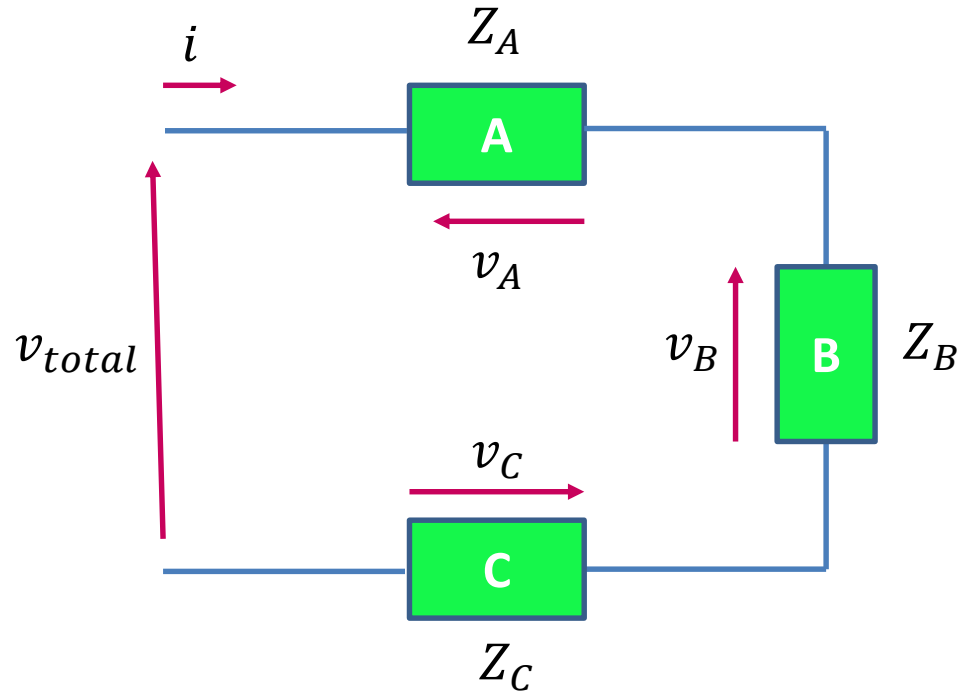

$$v_{total} = v_A + v_B + v_C$$

$$v_A = Z_A i, \quad v_B = Z_B i, \quad v_C = Z_C i$$


$$i = \frac{v_{total}}{Z_A + Z_B + Z_C}$$

$$v_A = \frac{Z_A}{Z_A + Z_B + Z_C} v_{total}, \quad v_B = \frac{Z_B}{Z_A + Z_B + Z_C} v_{total},$$


$$v_C = \frac{Z_C}{Z_A + Z_B + Z_C} v_{total}$$
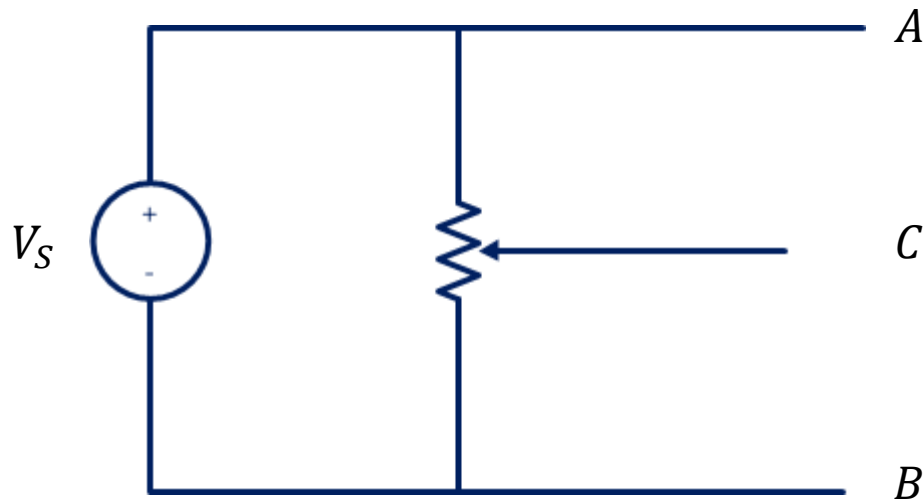
# Voltage divider circuits

- Voltage division principle is very useful as it can be used to produce a desired (or variable) output from a fixed supply.
- Potentiometers (a form of variable resistor) are commonly used for this purpose.



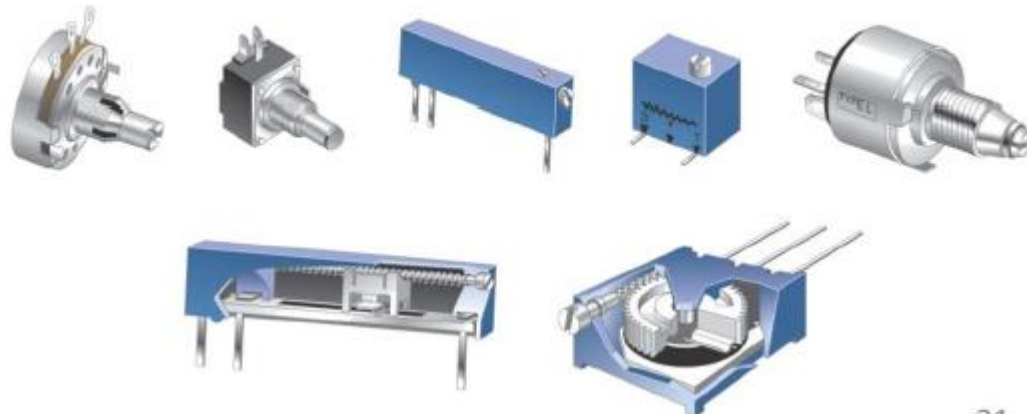
$$V_{BC} = \frac{R_{var}}{R_{Total}} \times V_S$$





# Current division principle

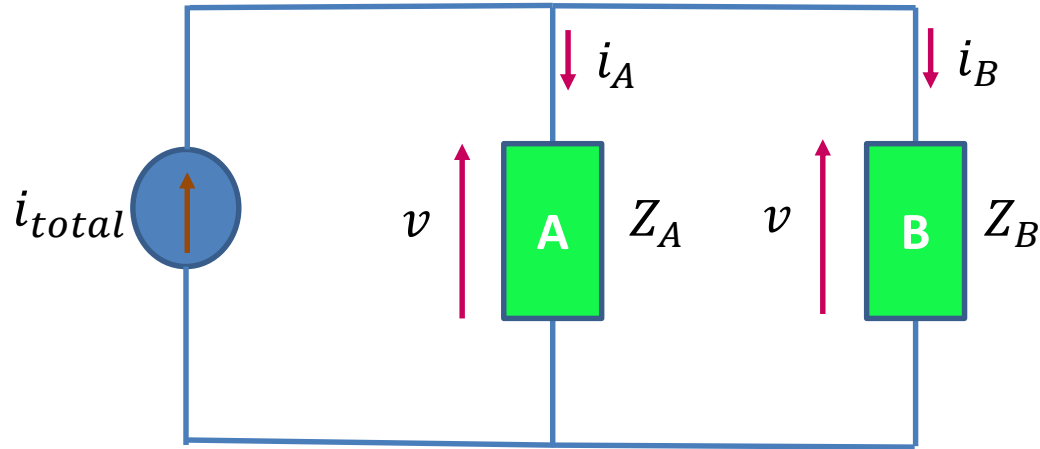


$$i_{total} = i_A + i_B$$
$$v = Z_{eq} i_{total} = \frac{Z_A Z_B}{Z_A + Z_B} i_{total}$$

$$i_A = \frac{v}{Z_A} = \frac{Z_B}{Z_A + Z_B} i_{total}$$

$$i_B = \frac{v}{Z_B} = \frac{Z_A}{Z_A + Z_B} i_{total}$$


# Example

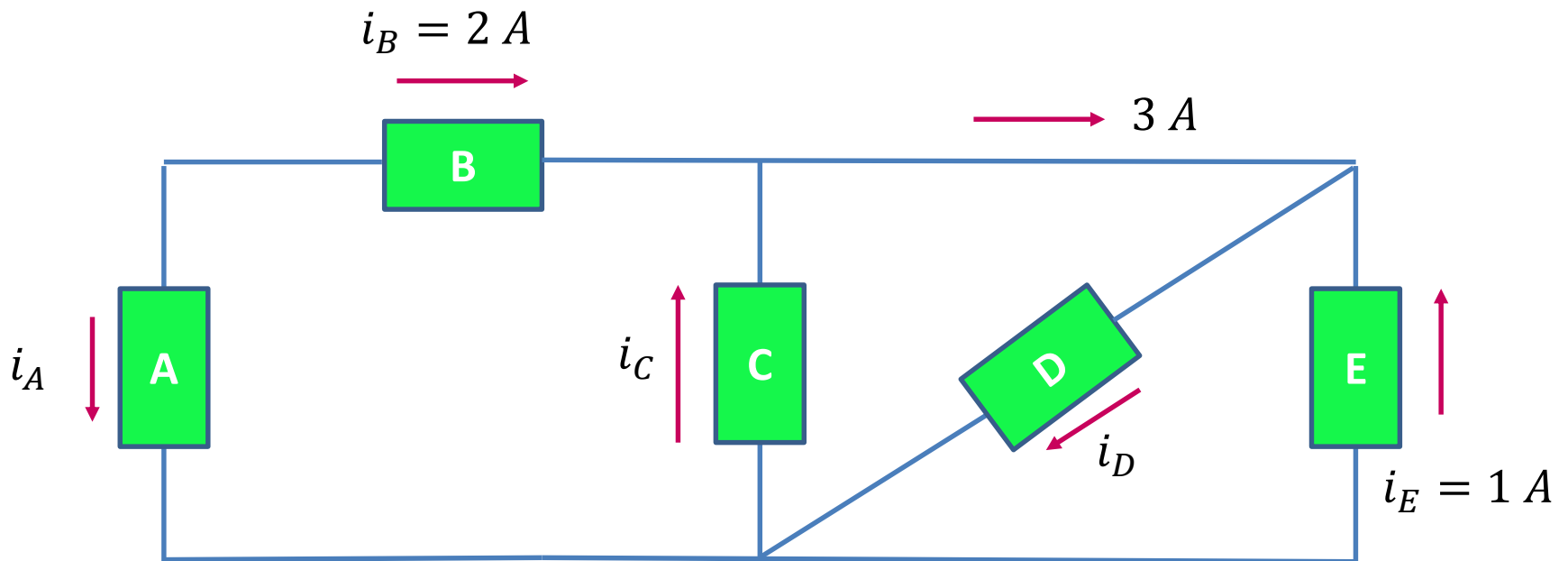- 1) Use KCL to find unknown currents in the circuit given below.




# Example

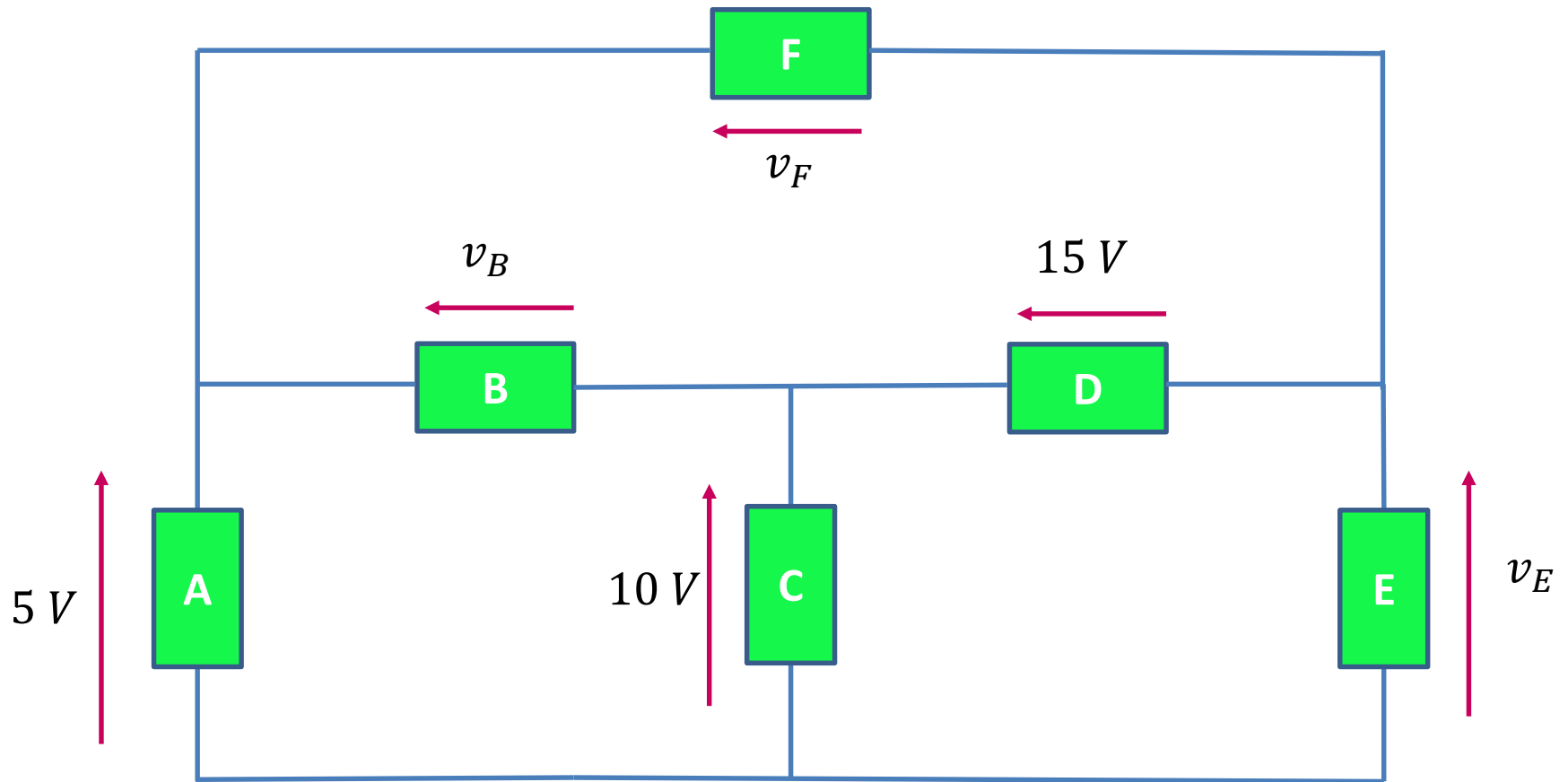2) Use KVL to find unknown voltages in the circuit given below.




# Example

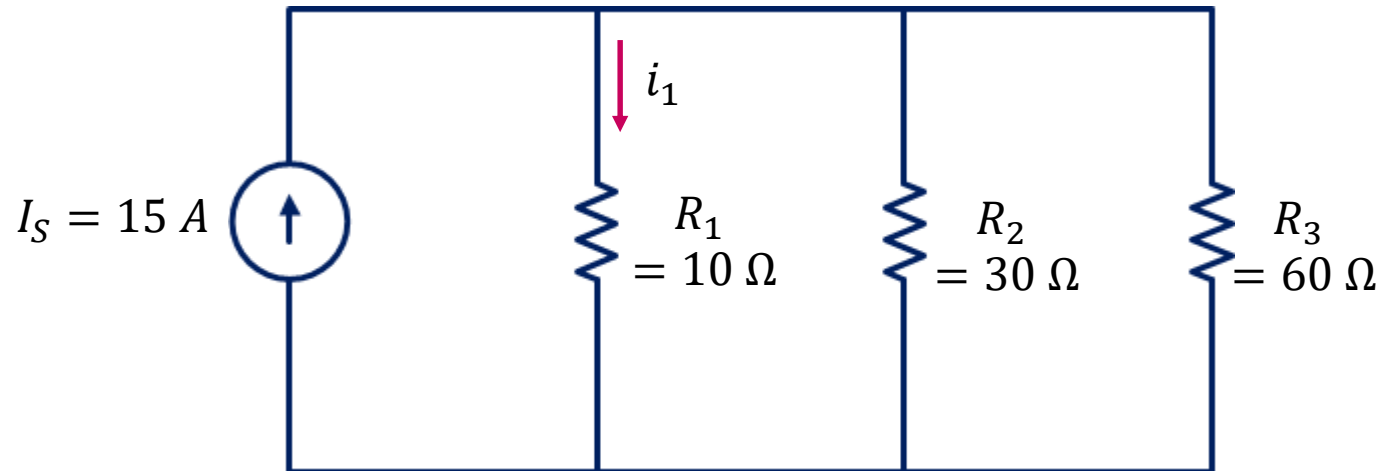3) Find the current  $i_1$  in the circuit given below.




# Example

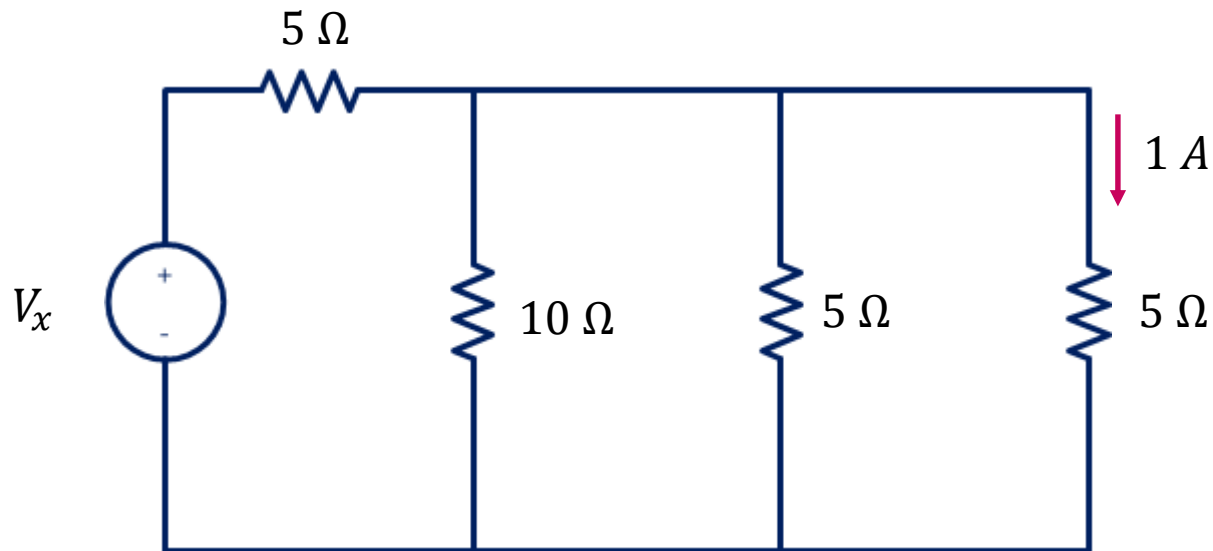4) Find the voltage  $V_x$  in the circuit given below.



# Example

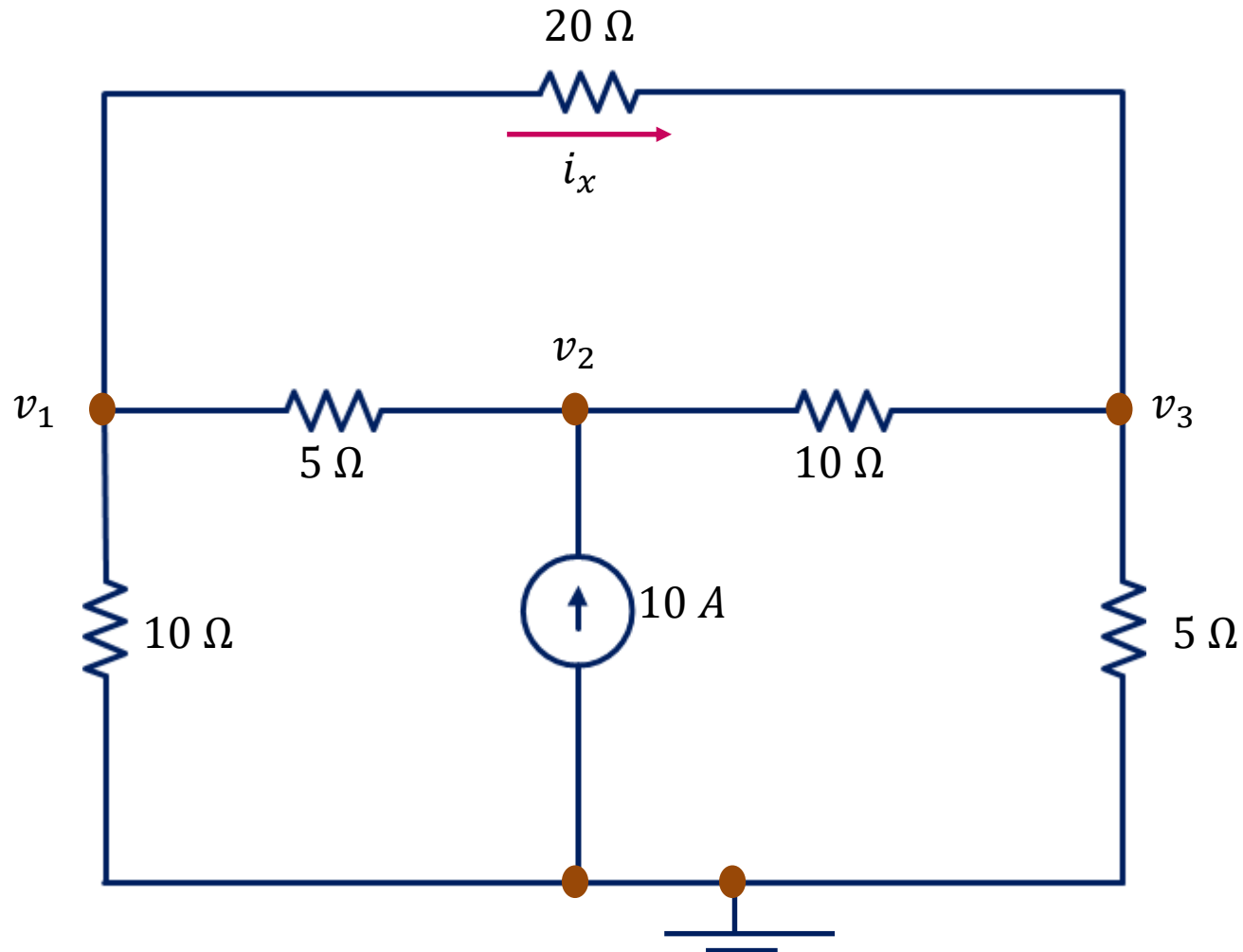5) Solve for the node voltages in the circuit below to calculate the current  $i_x$ .



## Example 5 solution

$$\begin{aligned}\frac{0 - v_1}{10} &= \frac{v_1 - v_3}{20} + \frac{v_1 - v_2}{5} && \rightarrow 7v_1 - 4v_2 - v_3 = 0 \\ 10 + \frac{v_1 - v_2}{5} &= \frac{v_2 - v_3}{10} && \rightarrow -2v_1 + 3v_2 - v_3 = 100 \\ \frac{v_2 - v_3}{10} + \frac{0 - v_3}{5} + \frac{v_1 - v_3}{20} &= 0 && \rightarrow v_1 + 2v_2 - 7v_3 = 0\end{aligned}$$

$$\begin{bmatrix} 7 & -4 & -1 \\ -2 & 3 & -1 \\ 1 & 2 & -7 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 100 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 45.45 \\ 72.72 \\ 27.27 \end{bmatrix} V$$

$$i_x = \frac{v_1 - v_3}{20} = \frac{45.45 - 27.27}{20}$$

**$i_x = 0.91 A$**