

# Chapter 2 – Basic Circuit Elements and Circuit Analysis

**W. D. Prasad**



# What is Electricity?

- (a) A quantity of either positive or negative charge.
- (b) A flow of charged particles.
- (c) An energy field produced by the motion of charged particles.
- (d) The force of attraction or repulsion between the charged particles.




# Charge

- The behaviour of electric/electronic components and circuits is determined by the motion of charge through the component/circuit.
- Electron is the fundamental charge carrier in electronics – the motion of electrons drives the functions and properties of all electronic components.
- The Bohr atom is useful in visualizing the atomic structure and understanding the charge.

**Nucleus consists of protons and neutrons**

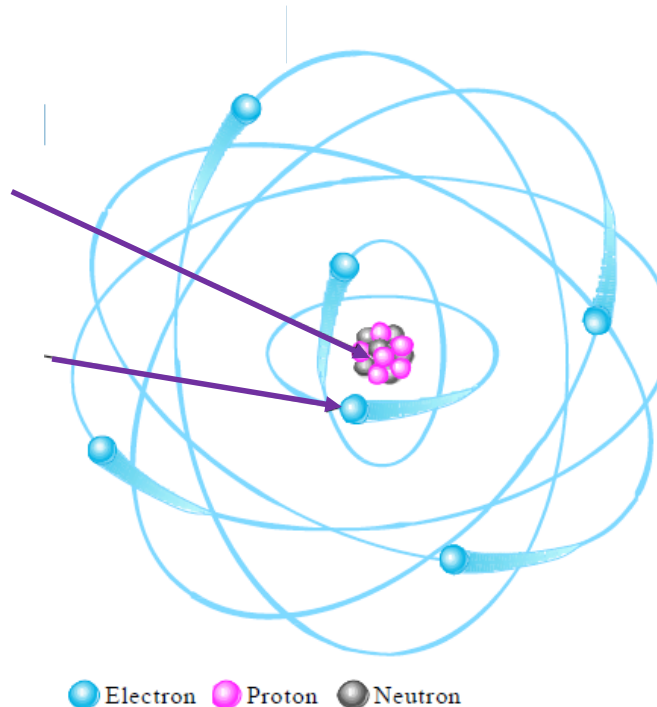**Negatively charged electrons are in discrete shells orbiting the nucleus**



# Charge

- Two kinds of charge: positive charge and negative charge.
- Charge is conserved.
- Charge is quantized.

$$Q = N \times (1.602 \times 10^{-19})$$

$Q$  = total charge

$N$  = Number of electrons


$1.602 \times 10^{-19}$  is the charge per electron

- The SI unit of charge is **Coulomb [C]**.
- One Coulomb of charge corresponds to  $6.25 \times 10^{18}$  number of electrons.
- Time invariant charge is usually referred to using the symbol  $Q$ , and the charge that may vary with time is usually referred to using the symbol  $q$ .

# Charge conduction

- The atomic structure of a material has a significant impact on the ability of electric charge to move through it.
- There are three categories of materials used in electrical and electronic circuits:
  - Conductors, insulators and semi-conductors

**The Copper Atom**

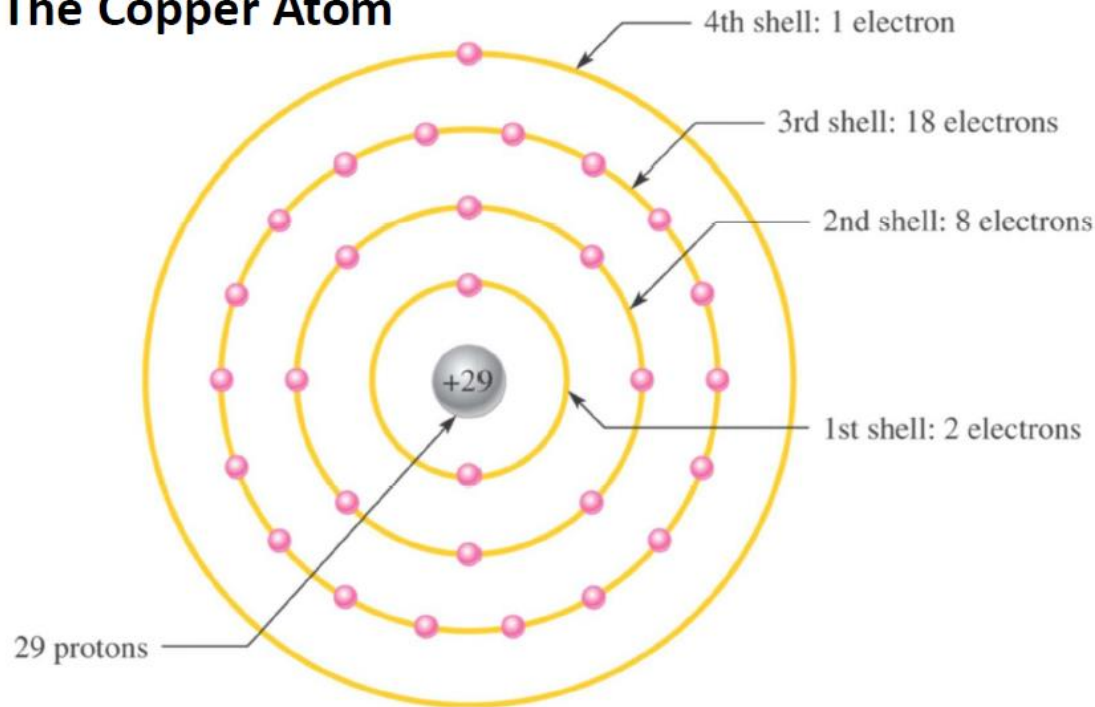


# Current

- An electric current is a flow of charge in a conductor.
- Current ( $I$ ) is defined as the amount of charge ( $Q$ ) in Coulomb that flows past a point in a unit time ( $t$ ) in second.

$$I = \frac{Q}{t}$$

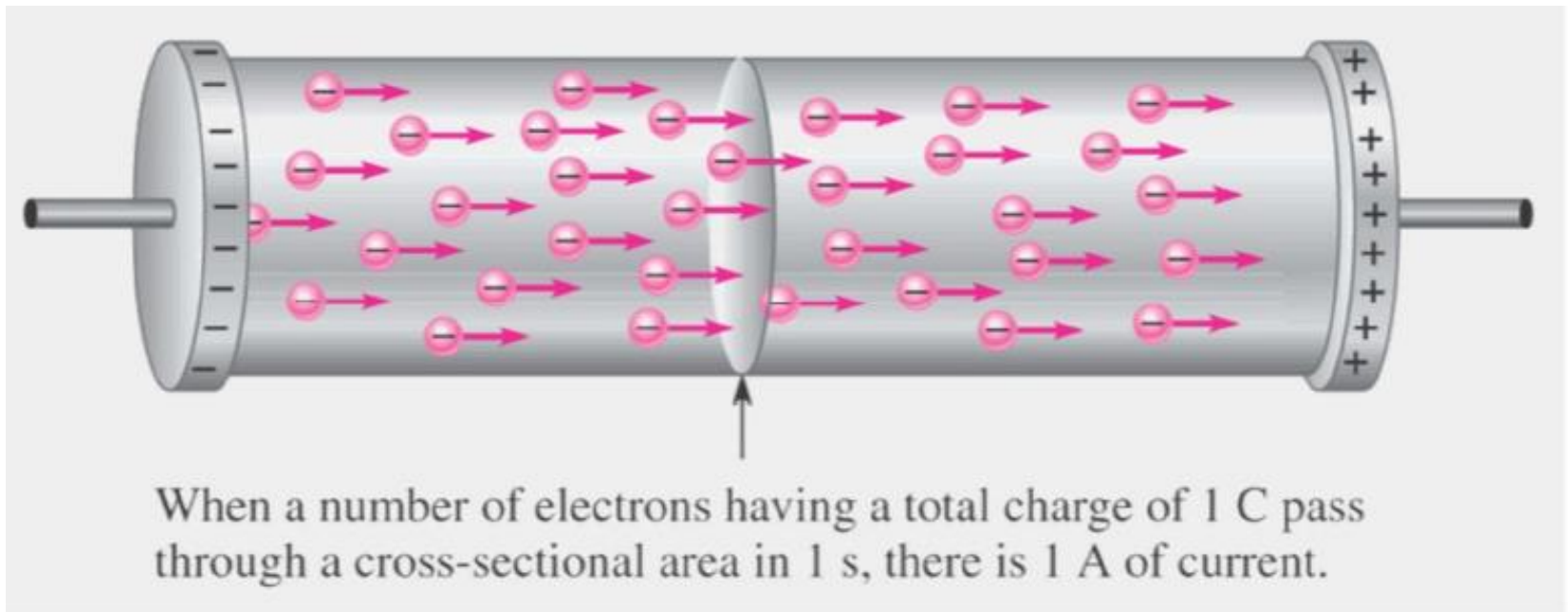- The SI unit of current is **Ampere (A)**.



# Current

- By convention, current flows from more positive to more negative potentials. This is known as conventional current.
- Electron flow is in the opposite direction of the conventional current.
- Time invariant current (direct current or DC) is referred to using the symbol  $I$ , current that varies with time (alternating current or AC) is usually referred to using the symbol  $i$ .

- **Example:**

- (1) If 300 C of charge flows through a minute, what is the current?

$$I = \frac{Q}{t} = \frac{300 \text{ (C)}}{60 \text{ (s)}} = 5 \text{ A}$$

- (2) If the current was 1.5 A, how much charge through in 10 seconds?

$$Q = It = 1.5 \times 10 = 15 \text{ C}$$

# Voltage

- Force is required to move a charge against the electric field (the electric field is a result of the forces of attraction or repulsion between charges).
- A difference of electrical potential, or potential difference, is defined by the work (W) which must be done to move a unit electric charge from one point to another.
- Potential difference is more commonly referred to as voltage.
- The SI unit for voltage (potential difference) is the **Volt (V)**.
- One volt is the potential difference between two points when one joule of energy is used to move one coulomb of charge from one point to the other.


$$V = \frac{E}{Q}$$

- Time invariant voltage is referred to using the symbol  $V$ , voltage that varies with time is referred to using the symbol  $v$ .
- In electrical circuits, one point is always nominated as a reference point (zero potential), called a common or ground point or simply ground.
- Normally a voltage (potential difference) must be referenced between two points.  $V_{AB} = V_A - V_B$



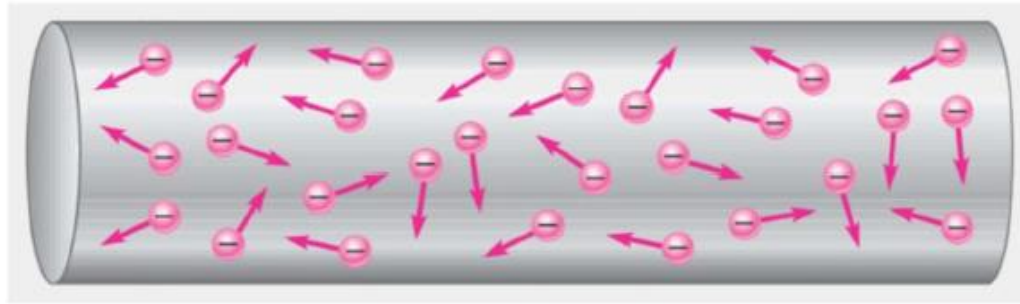
# Electron motion and current flow

- Consider a conductor of length  $L$  and cross-sectional area  $A$ . Electrons are the charge carriers.
- If there is no applied potential, the electrons will exhibit a degree of random motion due to thermal energy, but the average electron velocity will be zero. The electrons will be “localized”.




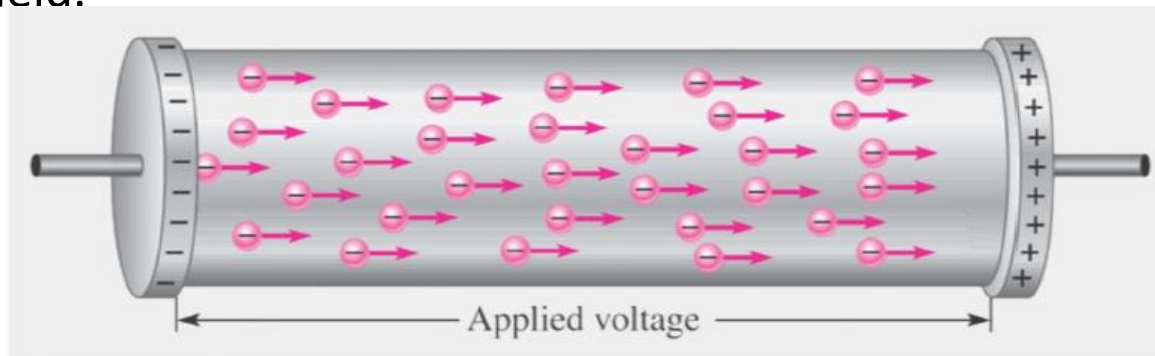- If a potential  $V$  is applied along the length of the conductor, the potential sets up an electric field.
- Electrons placed in this electric field will experience a force opposite direction to the electric field.


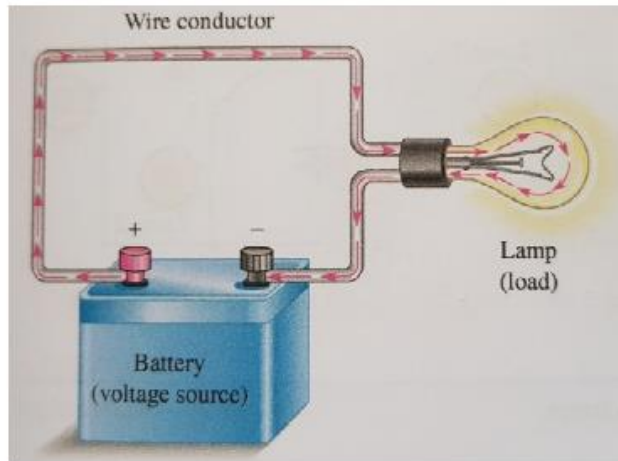
# Electrical circuits

- An electrical circuit essentially consists of different circuit elements connected in closed paths by wires.



Pictorial diagram



Schematic diagram

- An electrical circuit can be;
  - Closed circuit
  - Open circuit
  - Short circuit

# Energy and power

- Energy ( $E$  or  $W$ ) is used to do the work. Power ( $P$ ) is the rate at which the work is done (work done in unit time).

$$p = \frac{dw}{dt}$$
$$p = \frac{dw}{dq} \frac{dq}{dt} = vi$$
$$\mathbf{p = vi}$$


$$\mathbf{w = \int_{t_0}^t p dt = \int_{t_0}^t (vi) dt}$$

- Unit of Energy is **Joules (J)**. Unit of power is **Joules per second or Watt (W)**.
- Assume a constant voltage  $V$  applied across a resistor  $R$  gives current  $I$  in a time period of  $t$  seconds.

$$\text{Power (P)} = VI = I^2 R = \frac{V^2}{R}$$
$$\text{Energy (E)} = VIt = Pt$$

# Double subscript notation


- Current

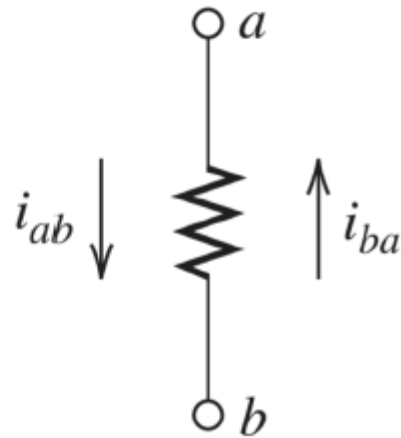

$i_{ab}$  indicates current flowing from  $a \rightarrow b$

$$i_{ab} = -i_{ba}$$

- Voltage

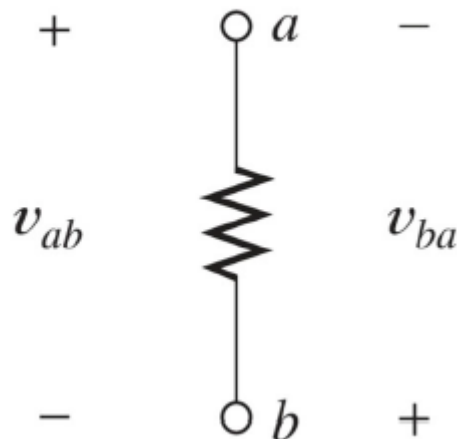

$v_{ab}$  indicates a voltage with a more positive polarity at point  $a$

$$v_{ab} = -v_{ba}$$

# Branch, node, loop, mesh in a circuit

- **Branch**

A branch represents a single element, such as a resistor or a battery. A branch is a two terminal element.

- **Node**


A node is the point connecting two or more branches. Usually a dot is used to represent a node.

- **Loop**

A loop is a closed path through a circuit in which no node is encountered more than once except for the same start/finish node.


- **Mesh**

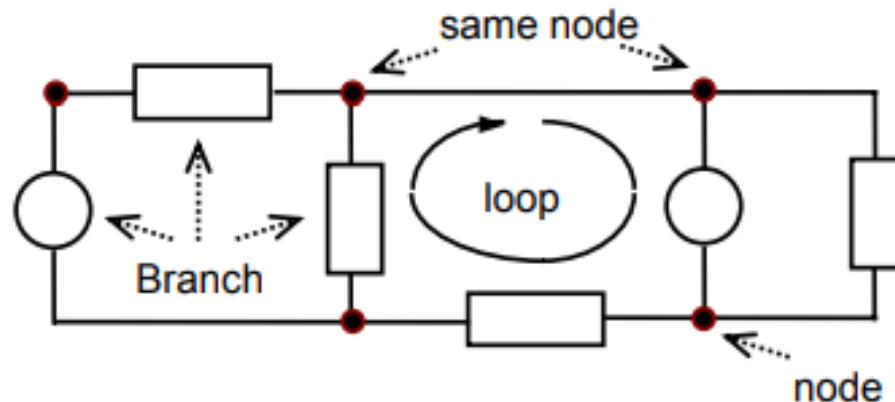A mesh is a loop without having other loops inside it.


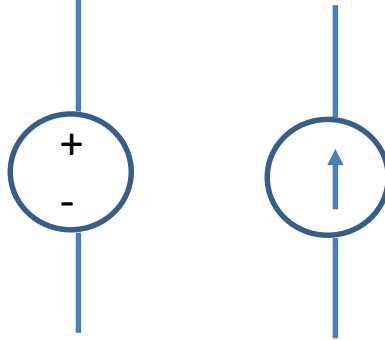
# Circuit elements


- Electric circuits consist of two basic types of elements.
  - Active elements
  - Passive elements
- An active circuit element is capable of generating electrical energy.
  - Voltage sources
  - Current sources



- A passive circuit element does not generate electrical energy. It either consumes electrical energy or stores it.
  - Resistors
  - Inductors
  - Capacitors
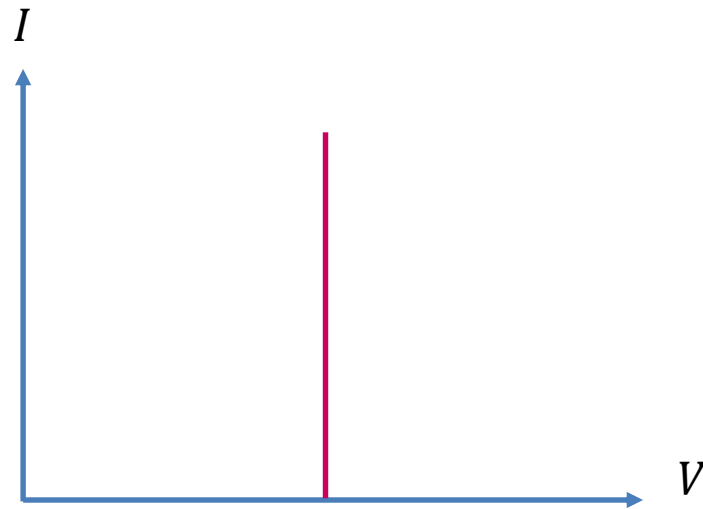
# Voltage sources

- Sources of voltage:
  - Batteries (electrochemical)
  - Solar cells (photo voltaic)
  - Generators (electromagnetic)
- Ideally, a voltage source can provide a constant voltage for any current required by a circuit.
- The current vs voltage curve for an ideal voltage source has a constant voltage for all current:



- In practice, ideal sources do not exist, but they can be closely approximated by actual sources.

# Resistors

- Resistance ( $R$ ) of a conductor in terms of the physical dimensions is given below:

$$R = \frac{\rho l}{A}$$

$\rho$  = resistivity,  $l$  = length,  $A$  = cross – sectional area

- The SI unit for resistance is the **Ohm ( $\Omega$ )**.
- If a voltage  $V$  is applied across a conductor, then a given current  $I$  will flow through the conductor ( $V \propto I$ ) – the proportionality constant is called resistance ( $R$ ).


$$R = \frac{V}{I} = \frac{\text{Voltage across the element}}{\text{Current passing through the element}}$$

- This resistance to current flow results from scattering of the electrons through collisions with atoms and impurities as they move through the conductor.
- A resistor is sized for the anticipated power.



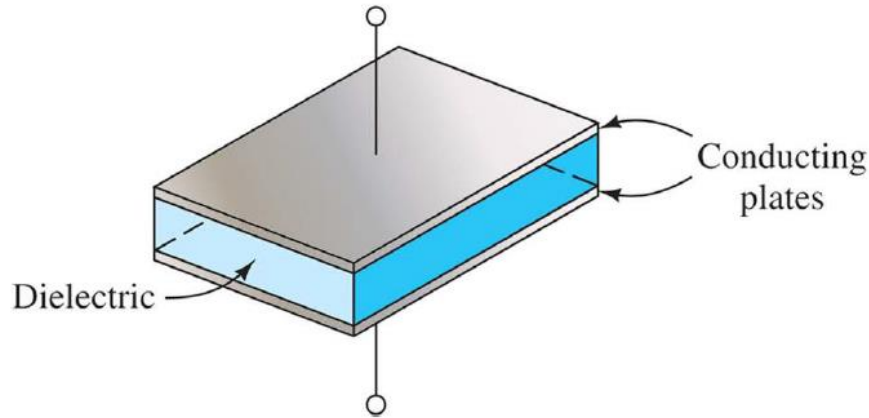
# Capacitors


- In its most basic form, a capacitor comprises two conductive plates separated by an insulating (dielectric) layer.




$$C = \frac{\epsilon A}{d}$$

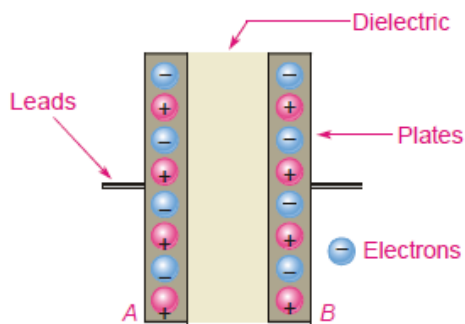

Initially uncharged

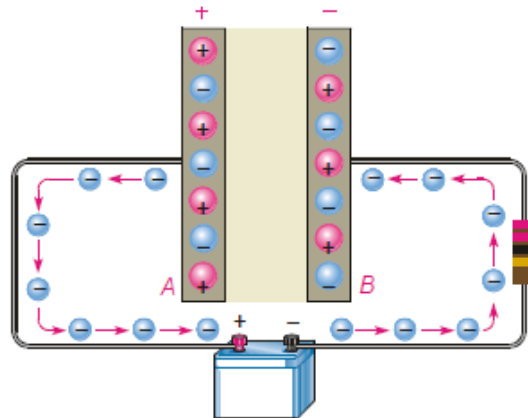

Charging

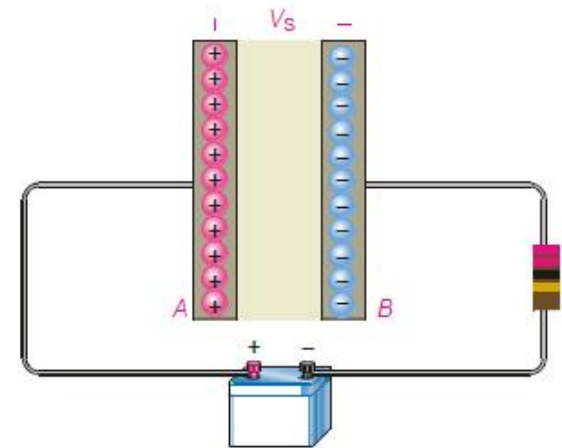

Fully charged

# Equations describing the capacitor operation

- In an ideal capacitor, the charge imbalance  $Q$  is proportional to the voltage  $V$  across the plates.

$$Q = CV$$

$C$  is the capacitance.

- Unit of capacitance is Farad (F).
- The capacitance  $C$  is a fixed constant. Therefore, the current  $i$  passing through the capacitor and voltage  $v$  across the capacitor are related as follows.

$$q = CV \rightarrow \frac{dq}{dt} = C \frac{dv}{dt}$$

$$i = C \frac{dv}{dt}$$


- Energy stored in the capacitor:  
Assume voltage across an Initially uncharged capacitor rises to  $V$  during a time period of  $t$  seconds.

$$e = \int_0^t p dt = \int_0^t (vi) dt = C \int_0^t v dv$$


$$E = \frac{1}{2} CV^2$$
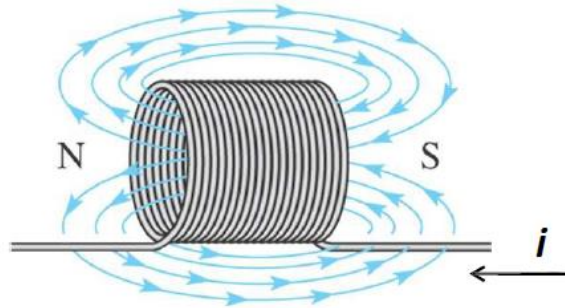
# Inductors

- When a length of wire is formed into a coil, it becomes a basic inductor.
  - When there is current in the inductor, a magnetic field is created.
- Any change in current causes the magnetic field to change, this in turn induces a voltage across the inductor that opposes the original change in current.



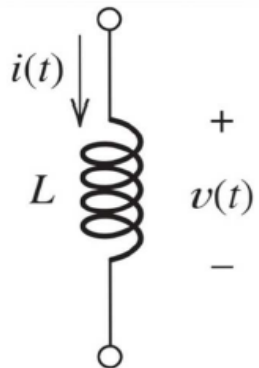- For an ideal inductor, the voltage is proportional to the time rate of change of the current and the polarity is such as to oppose the change in current.
- The constant of proportionality is called inductance,  $L$ .




$$v = L \frac{di}{dt}$$

# Energy stored in an inductor

- Assume current through an inductor rises to  $i$  during a time period of  $t$  seconds.

$$e = \int_0^t p dt = \int_0^t (vi) dt = L \int_0^t i di$$
$$E = \frac{1}{2} Li^2$$

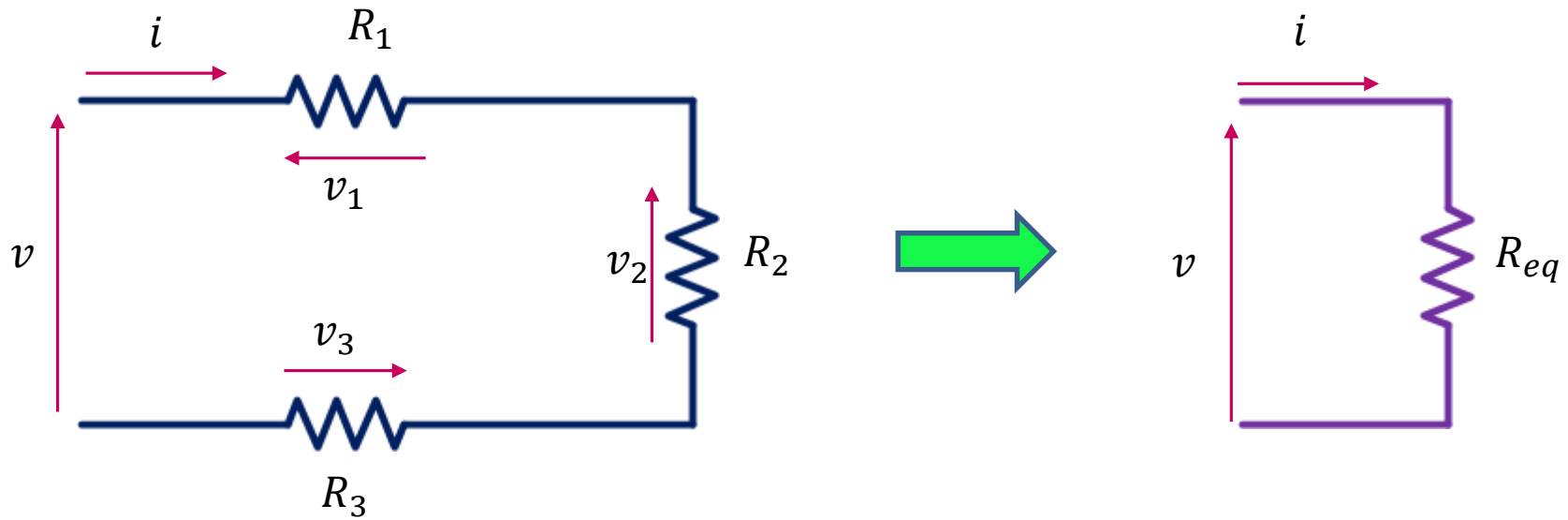
# Equivalence resistance: series connection



$$\begin{aligned}v &= v_1 + v_2 + v_3 \\v_1 &= iR_1, v_2 = iR_2, v_3 = iR_3 \\v &= iR_{eq} \\R_{eq} &= R_1 + R_2 + R_3\end{aligned}$$

$$R_{eq} = \sum_{i=1}^n R_i$$
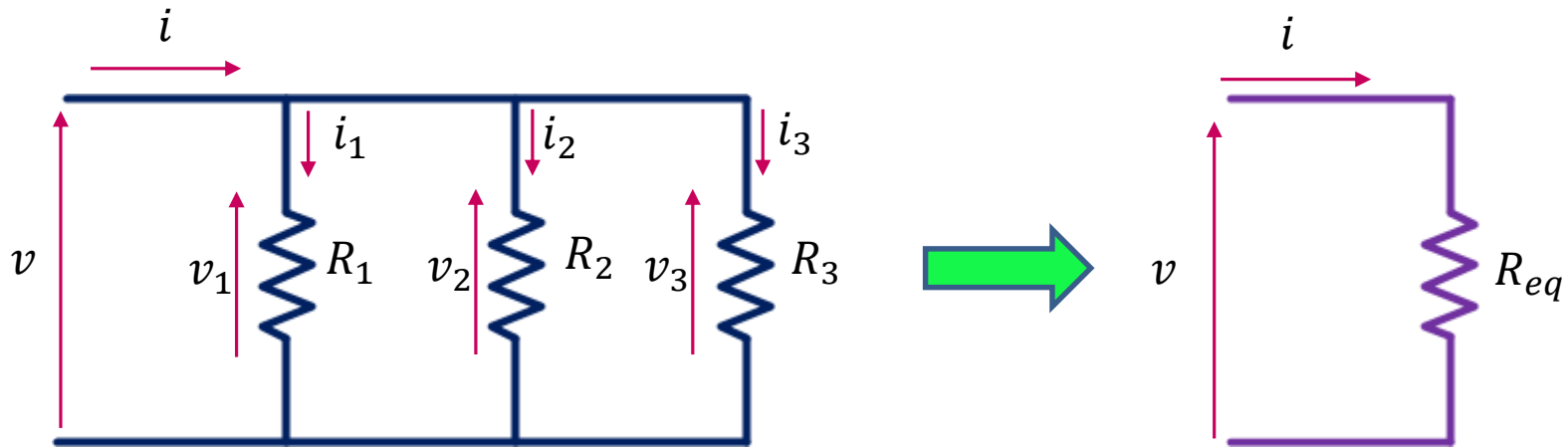
# Equivalence resistance: shunt connection



$$i = i_1 + i_2 + i_3$$

$$v_1 = v_2 = v_3 = v$$

$$v_1 = i_1 R_1, v_2 = i_2 R_2, v_3 = i_3 R_3$$


$$v = i R_{eq}$$

$$\frac{v}{R_{eq}} = \frac{v}{R_1} + \frac{v}{R_2} + \frac{v}{R_3}$$

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$R_{eq} = \frac{1}{\sum_i^n \frac{1}{R_i}}$$
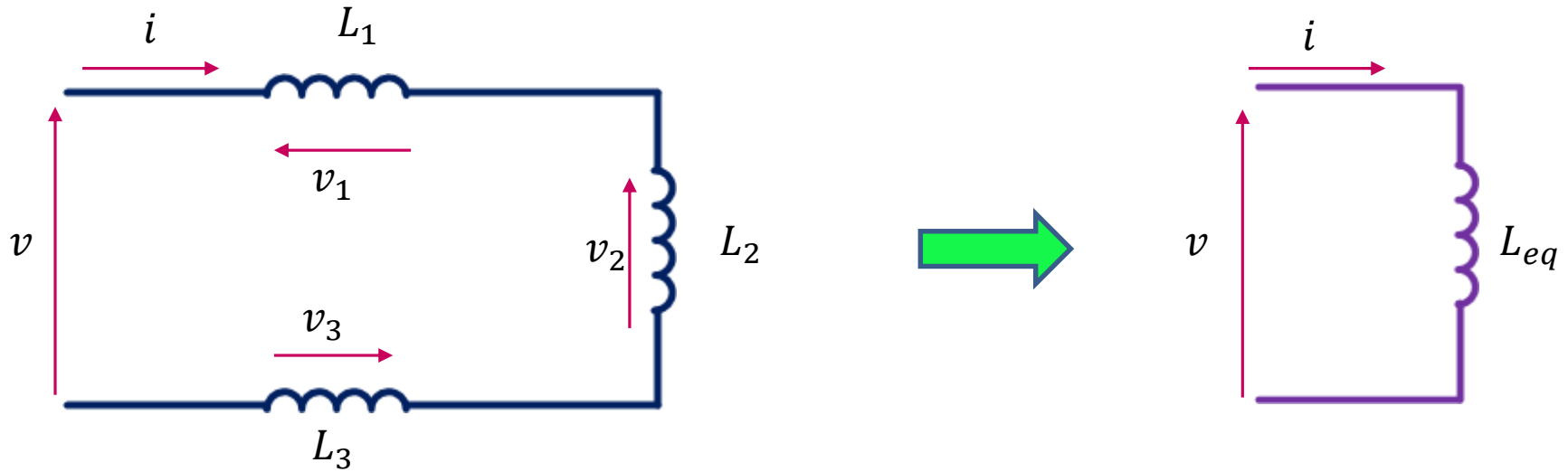
# Equivalence inductance: series connection



$$v = v_1 + v_2 + v_3$$


$$v_1 = L_1 \frac{di}{dt}, v_2 = L_2 \frac{di}{dt}, v_3 = L_3 \frac{di}{dt}$$

$$v = L_{eq} \frac{di}{dt}$$

$$L_{eq} = L_1 + L_2 + L_3$$

$$L_{eq} = \sum_{i=1}^n L_i$$
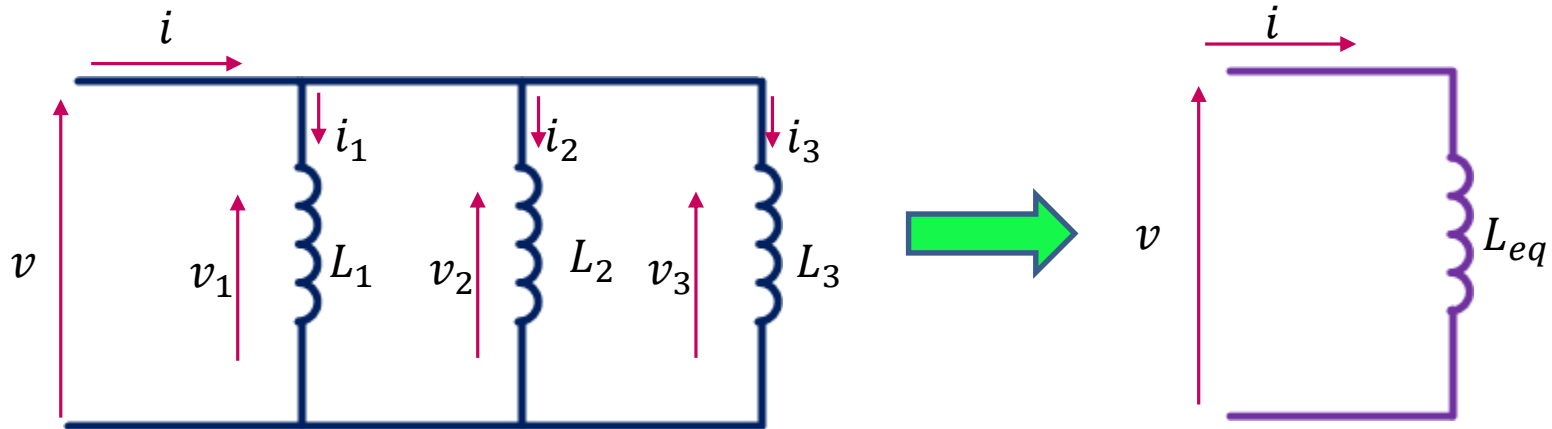
# Equivalence inductance: shunt connection



$$i = i_1 + i_2 + i_3$$

$$v_1 = v_2 = v_3 = v$$

$$v_1 = L_1 \frac{di}{dt}, v_2 = L_2 \frac{di}{dt}, v_3 = L_3 \frac{di}{dt}, v = L_{eq} \frac{di}{dt}$$


$$\frac{v}{L_{eq}} = \frac{v}{L_1} + \frac{v}{L_2} + \frac{v}{L_3}$$

$$L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}}$$

$$L_{eq} = \frac{1}{\sum_i^n \frac{1}{L_i}}$$


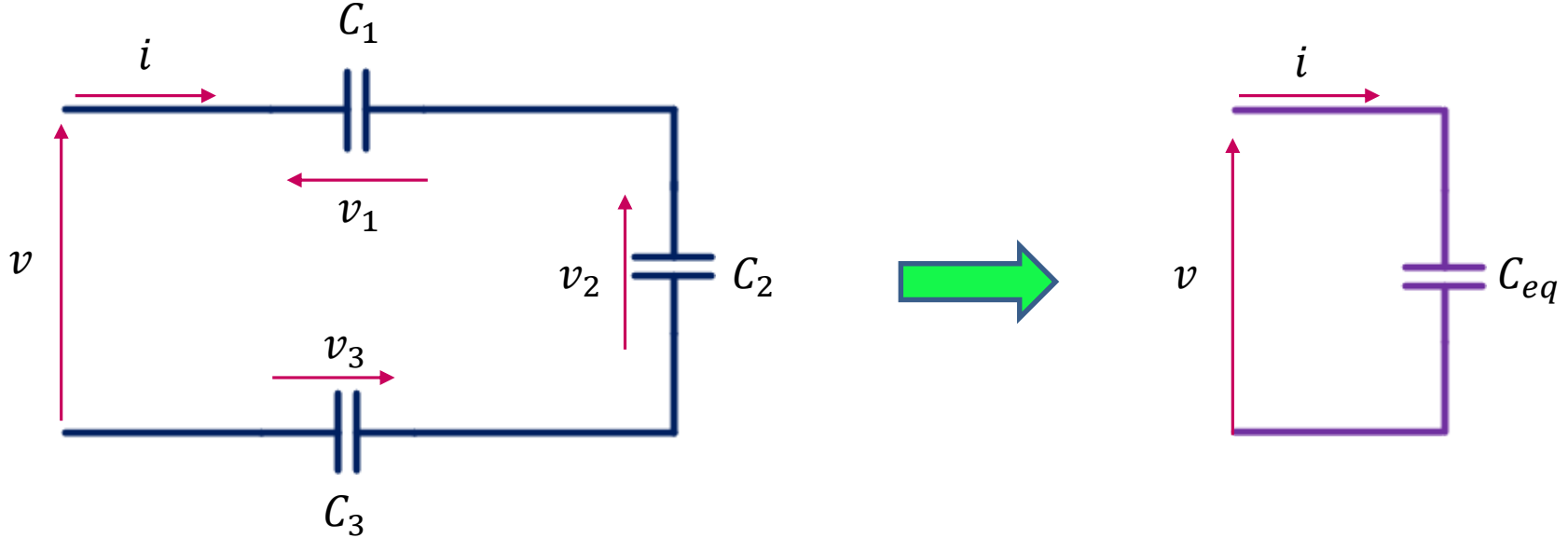
# Equivalence capacitance: series connection



$$v = v_1 + v_2 + v_3$$


$$q = Cv \rightarrow v_1 = \frac{q}{C_1}, v_2 = \frac{q}{C_2}, v_3 = \frac{q}{C_3}, v = \frac{q}{C_{eq}}$$

$$\frac{q}{C_{eq}} = \frac{q}{C_1} + \frac{q}{C_2} + \frac{q}{C_3}$$

$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$

$$C_{eq} = \frac{1}{\sum_i^n \frac{1}{C_i}}$$
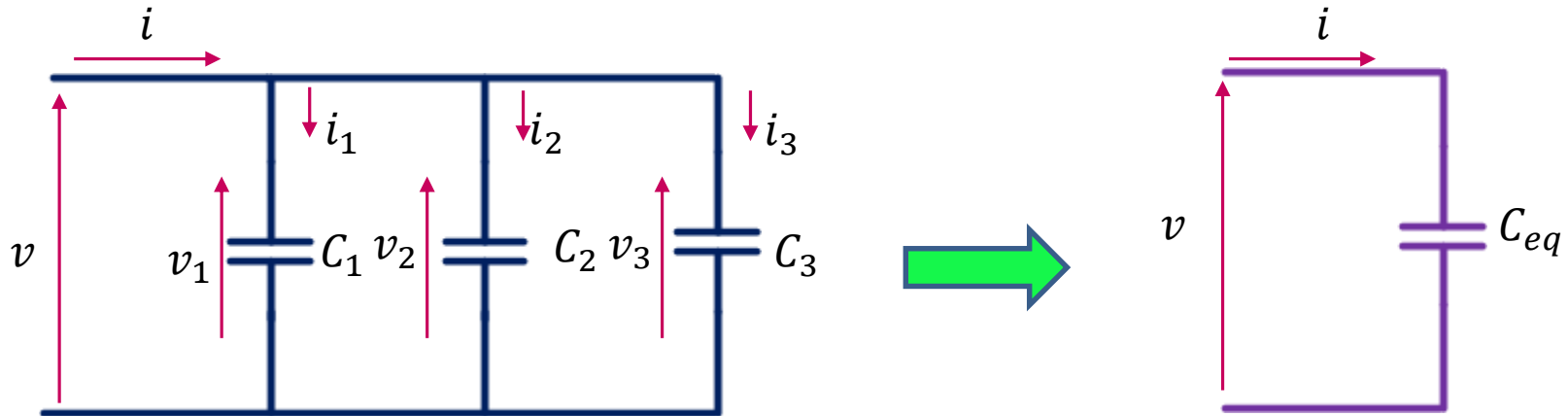
# Equivalence capacitance: shunt connection



$$i = i_1 + i_2 + i_3$$

$$v_1 = v_2 = v_3 = v$$

$$q = Cv \rightarrow i = C \frac{dv}{dt}$$

$$C_{eq} \frac{dv}{dt} = C_1 \frac{dv_1}{dt} + C_2 \frac{dv_2}{dt} + C_3 \frac{dv_3}{dt}$$

$$C_{eq} = C_1 + C_2 + C_3$$

$$C_{eq} = \sum_{i=1}^n C_i$$